

# Electricity

## Electric Current

- **Electric current** is expressed as the amount of charge flowing through a particular area in unit time.
- Quantitatively, **electric current** is defined as the rate of flow of electric charge.

$$\text{Current, } I = \frac{\text{Charge flowing (Q)}}{\text{Time taken (t)}}$$

- The S.I. unit of current is **ampere (A)**, where 1 ampere = 1 coulomb/second.
- $1 \text{ mA} = 10^{-3} \text{ A}$ ,  $1 \mu \text{ A} = 10^{-6} \text{ A}$
- The conventional direction of electric current is the one in which positive charges move orderly.

## Electric Potential Different

- Electric potential difference (pd) between two points in an electric circuit, carrying some current, is the amount of work done to move a unit charge from one point to another.



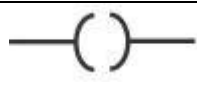
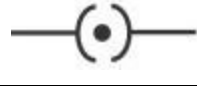

$$\text{Potential difference, pd} = \frac{\text{Work done (W)}}{\text{Quantity of charge moved (Q)}}$$

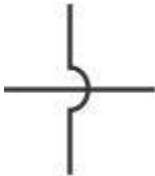
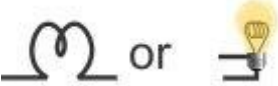

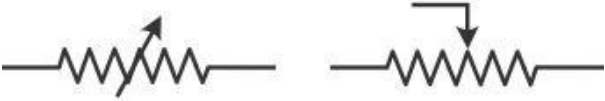


- The S.I. unit of pd is **volt (V)**, where 1 volt = 1 joule/coulomb.

## Electric Circuit

A continuous conducting path between the terminals of a source of electricity is called an **electric circuit**.

- A drawing showing the way various electric devices are connected in a circuit is called a **circuit diagram**.
- Some commonly used circuit elements are given below:

Sr. No.	Element	Symbol
1	An electric cell	
2	A battery	
3	Plug key or switch (open)	
4	Plug key or switch (closed)	
5	A wire joint	

6	Wires crossing without joining	
7	Bulb	
8	Resistor	
9	Variable resistor or Rheostat	
10	Ammeter	
11	Voltmeter	

## Ohm's law

---

- According to Ohm's law, the current (I) flowing through a conductor is directly proportional to the potential difference (V) across its ends, provided its physical conditions remain the same.

$$V \propto I$$

$$V/I = \text{Constant}$$

$$V/I = R$$

$$V = IR$$

where R is a constant of proportionality called **resistance** of the conductor.

- Resistance** is the property of a conductor to resist the flow of charges through it.
- The S.I. unit of resistance is **ohm ( $\Omega$ )**.

$$\text{From } R = \frac{V}{I}, 1 \text{ ohm} = 1 \text{ volt/ampere}$$

## Resistivity

---

- The resistance of a conductor is directly proportional to its length (l) and inversely proportional to its area of cross section (A).

$$R \propto l/A$$

$$R = \rho l/A$$

where  $\rho$  is a constant of proportionality called **specific resistance** or **resistivity** of the material of the conductor.

- The S.I. unit of resistivity is **ohm metre ( $\Omega \text{ m}$ )**.

## Combination of Resistances

---

### Resistances in Series

- The current flowing through each resistance is the same.
- The potential difference across the ends of the series combination is distributed across the resistances.
- The equivalent resistance ( $R_s$ ) of a series combination containing resistances  $R_1, R_2, R_3, \dots$  is  $R_s = R_1 + R_2 + R_3 + \dots$
- The equivalent resistance is greater than the greatest resistance in the combination.

### Resistances in Parallel

- The potential difference across each resistance is the same and is equal to the potential difference across the combination.
- The main current divides itself, and a different current flows through each resistance.
- The equivalent resistance ( $R_p$ ) of a parallel combination containing resistances  $R_1, R_2, R_3, \dots$  is given by  $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
- The equivalent resistance is lesser than the least of all the resistances in the combination

### Heating Effect of Electric Current

- The effect of electric current due to which heat is produced in a conductor, when current passes through it, is called the heating effect of electric current.
- The total work ( $W$ ) done by the current in an electric circuit is called **electric energy** and is given as

$$W = VIt = I^2Rt$$

$$W = V^2 t / R$$

This energy is exhibited as heat. Thus, we have  $H = VIt = I^2Rt$ .

This is called **Joule's Law of Heating**, which states that the heat produced in a resistor is directly proportional to the

- Square of the current in the resistor
- Resistance of the resistor
- Time for which the current flows through the resistance

### Practical Applications of the Heating Effects of Electric Current

- Electrical appliances like laundry iron, toaster, oven, kettle and heater are some devices based on Joule's Law of Heating.
- The concept of electric heating is also used to produce light, as in an electric bulb.
- Another application of Joule's Law of Heating is the fuse used in electric circuits.

## Electric Power

- Electric power is the rate at which electrical energy is produced or consumed in an electric circuit  
 $P = VI = I^2R$   
 $P = V^2/R$
- The **S.I. unit** of power is **watt (W)**.
- One watt of power is consumed when 1 A of current flows at a potential difference of 1 V.  
 The commercial unit of electric energy is **kilowatt hour (kWh)**, commonly known as a **unit**.  
 $1 \text{ kWh} = 3.6 \text{ MJ}$

### NUMERICAL PROBLEMS

1. Find the charge if the number of electrons is  $4 \times 10^{-18}$ .
2. Find the number of electrons constituting one coulomb of charge.
3. How much work done in moving a charge of 3 coulombs from a point at 118 V to a point at 128 volt?
4. How much work done in moving a charge of 2C across two points having a potential difference of 12V?
5. Calculate the amount of work done to carry 4C from a point at 100 V to a point at 120 volt?
6. How much work will be done in bringing a charge of  $2 \times 10^{-3}$  coulombs from infinity to a point P at which the potential is 5 V?
7. How much work will be done in bringing a charge of  $3 \times 10^{-2}$  coulombs from infinity to a point P at which the potential is 20 V?
8. How much energy is given to each coulomb of charge passing through a 6V battery?
9. How much energy is transferred by a 12 V power supply to each coulomb of charge which it moves around a circuit?
10. What is the potential difference between the terminals of a battery if 250 joules of work is required to transfer 20 coulombs of charge from one terminal of battery to the other?